

Farzin Asadi

Digital Circuits Laboratory Manual

Synthesis Lectures on Electrical Engineering

This series of short books covers a broad spectrum of titles of interest in electrical engineering that may not specifically fit within another series. Books will focus on fundamentals, methods, and advances of interest to electrical and electronic engineers.

Farzin Asadi

Digital Circuits Laboratory Manual

 Springer

Farzin Asadi
Department of Electrical and Electronics
Engineering
Maltepe University
Istanbul, Türkiye

ISSN 1559-811X ISSN 1559-8128 (electronic)
Synthesis Lectures on Electrical Engineering
ISBN 978-3-031-41515-9 ISBN 978-3-031-41516-6 (eBook)
<https://doi.org/10.1007/978-3-031-41516-6>

© The Editor(s) (if applicable) and The Author(s), under exclusive license to Springer Nature Switzerland AG 2024

This work is subject to copyright. All rights are solely and exclusively licensed by the Publisher, whether the whole or part of the material is concerned, specifically the rights of translation, reprinting, reuse of illustrations, recitation, broadcasting, reproduction on microfilms or in any other physical way, and transmission or information storage and retrieval, electronic adaptation, computer software, or by similar or dissimilar methodology now known or hereafter developed.

The use of general descriptive names, registered names, trademarks, service marks, etc. in this publication does not imply, even in the absence of a specific statement, that such names are exempt from the relevant protective laws and regulations and therefore free for general use.

The publisher, the authors, and the editors are safe to assume that the advice and information in this book are believed to be true and accurate at the date of publication. Neither the publisher nor the authors or the editors give a warranty, expressed or implied, with respect to the material contained herein or for any errors or omissions that may have been made. The publisher remains neutral with regard to jurisdictional claims in published maps and institutional affiliations.

This Springer imprint is published by the registered company Springer Nature Switzerland AG
The registered company address is: Gewerbestrasse 11, 6330 Cham, Switzerland

Paper in this product is recyclable.

*In loving memory of my father Moloud Asadi and
my mother Khorshid Tahmasebi, always on my
mind, forever in my heart.*

Preface

Digital technology pervades almost everything in our daily lives. For example, cell phones and other types of wireless communications, laptops, television, radio, process controls, automotive electronics, consumer electronics, and aircraft navigation, to name only a few applications that depend heavily on digital electronics.

A strong grounding in the fundamentals of digital technology will prepare you for the highly skilled jobs of the future. Understanding the core fundamentals is very important since it enables you to go anywhere.

This book can be used as a laboratory manual for any standard textbook on digital electronics. You can make the circuits on breadboard or you can use a simulation software like Proteus® to simulate the circuits.

This book is composed of 11 chapters. Here is a brief summary of each chapter:

Chapter 1 is an Introduction to Digital Systems.

Chapter 2 contains experiments related to Logic Gates and Combinational Logic Circuits.

Chapter 3 contains experiments related to Digital Arithmetic.

Chapter 4 contains experiments related to Multiplexers and De-multiplexers.

Chapter 5 contains experiments related to Encoders and Decoders.

Chapter 6 contains experiments related to Display Information on Seven Segments.

Chapter 7 contains experiments related to Latches, Flip Flops and Shift Registers.

Chapter 8 contains experiments related to Frequency Division with Flip Flops.

Chapter 9 contains experiments related to Counter Circuits.

Chapter 10 contains experiments related to Oscillator Circuits.

Chapter 11 contains experiments related to Analog-to-Digital and Digital-to-Analog Conversion.

I hope that this book will be useful to the readers, and I welcome comments on the book.

Istanbul, Türkiye

Farzin Asadi

Contents

| | | |
|----------|---|-----------|
| 1 | An Introduction to Digital Systems | 1 |
| 1.1 | Introduction | 1 |
| 1.2 | Logic Technologies | 1 |
| 1.3 | Transistor Transistor Logic (TTL) | 1 |
| 1.4 | Complementary Metal Oxide Semiconductor (CMOS) | 5 |
| 1.5 | Emitter Coupled Logic (ECL) | 6 |
| 1.6 | Pin Numbering | 6 |
| 1.7 | CMOS and TTL Logic Levels | 7 |
| 1.8 | Schematic Conventions | 8 |
| 1.9 | Generation of High and Low Signals | 9 |
| 1.10 | Bouncing Problem | 11 |
| 1.11 | De-bouncing | 11 |
| 1.12 | Output Status Monitoring | 16 |
| 1.13 | Measurement with Cell Phones | 18 |
| 1.14 | Power Supply for Digital Circuits | 19 |
| 1.15 | Open Collector Gates | 20 |
| | References for Further Study | 24 |
| 2 | Logic Gates and Combinational Logic Circuits | 25 |
| 2.1 | Introduction | 25 |
| 2.2 | Implementation of Logic Gates with Diode and Transistor | 28 |
| 2.3 | Behavior of Inverter (Not Gate) with Schmitt Trigger Inputs | 31 |
| 2.4 | Measurement of Lower and Upper Trigger Points with Potentiometer | 34 |
| 2.5 | Behavior of Inverter Without Schmitt Trigger Inputs | 35 |
| 2.6 | Measurement of Output Impedance of Gates in High State | 38 |
| 2.7 | Measurement of Output Impedance of Gates in Low State | 39 |
| 2.8 | Connecting a Relay to Logic Gates | 41 |
| 2.9 | Simple Logic Analyzer | 43 |
| 2.10 | Buffer ICs | 44 |

| | | |
|----------|--|------------|
| 2.11 | Bus Transceiver ICs | 47 |
| 2.12 | Behavior of Basic Logic Gates | 53 |
| 2.13 | De Morgan's Rule | 58 |
| 2.14 | Implementation of Basic Logic Gates with NAND Gate | 60 |
| 2.15 | Implementation of Basic Logic Gates with NOR Gate | 63 |
| 2.16 | Conversion of Sine Wave to Square Wave | 64 |
| | References for Further Reading | 66 |
| 3 | Digital Arithmetic | 67 |
| 3.1 | Introduction | 67 |
| 3.2 | Adder IC | 67 |
| 3.3 | BCD Adder Circuit | 71 |
| 3.4 | 2-Bit Multiplier | 74 |
| 3.5 | Magnitude Comparator IC | 76 |
| 3.6 | ALU IC | 80 |
| | References for Further Study | 80 |
| 4 | Multiplexer and De-multiplexer | 81 |
| 4.1 | Introduction | 81 |
| 4.2 | Multiplexer | 81 |
| 4.3 | De-multiplexer | 86 |
| 4.4 | Analog Multiplexer and De-multiplexer | 90 |
| 4.5 | Measurement of Switch Resistance | 97 |
| 4.6 | Analog Switch | 100 |
| 4.7 | Digitally Controlled Voltage Gain | 101 |
| | References for Further Study | 103 |
| 5 | Encoder and Decoder | 105 |
| 5.1 | Introduction | 105 |
| 5.2 | Decimal to Binary Coded Decimal (BCD) Priority Encoder | 105 |
| 5.3 | Reading a Keypad | 108 |
| 5.4 | 8-Line to 3-Line Binary (Octal) Priority Encoder | 109 |
| 5.5 | 3 × 8 Decoder | 111 |
| 5.6 | BCD to Decimal Decoder (TTL IC) | 115 |
| 5.7 | BCD to Decimal Decoder (CMOS IC) | 118 |
| 5.8 | BCD-to-Binary and Binary-to-BCD Converters | 121 |
| | References for Further Study | 124 |
| 6 | Display Information on Seven Segments | 125 |
| 6.1 | Introduction | 125 |
| 6.2 | TTL BCD to Common Cathode 7-Segment Decoder | 126 |
| 6.3 | Counter from 0 to 9 | 129 |
| 6.4 | TTL BCD to Common Anode 7-Segment Decoder | 130 |

| | | |
|----------|--|------------|
| 6.5 | CMOS BCD to 7-Segment Decoder | 132 |
| 6.6 | Binary to BCD and BCD to Binary Converter IC | 133 |
| | References for Further Study | 135 |
| 7 | Latch, Flip Flop and Shift Register | 137 |
| 7.1 | Introduction | 137 |
| 7.2 | Commonly Used JK Flip Flops | 137 |
| 7.3 | Commonly Used D Flip Flops | 141 |
| 7.4 | Commonly Used D Type Data Latches | 144 |
| 7.5 | Commonly Used SR Latch | 145 |
| 7.6 | SR Latch with Transistors | 145 |
| 7.7 | Active High SR Latch | 147 |
| 7.8 | Active Low SR Latch | 149 |
| 7.9 | De-bouncing with SR Latch | 151 |
| 7.10 | Behavior of JK Flip Flops | 153 |
| 7.11 | Conversion of JK Flip Flop to T Flip Flop | 156 |
| 7.12 | Conversion of JK Flip Flop to D Flip Flop | 158 |
| 7.13 | Conversion of D Flip Flop to T Flip Flop | 160 |
| 7.14 | De-bouncing with D Flip Flops | 162 |
| 7.15 | 4-Bit Latch | 163 |
| 7.16 | 8-Bit Latch | 169 |
| 7.17 | Edge Detector Circuits | 170 |
| 7.18 | Edge Detection with D Flip Flops | 172 |
| 7.19 | Shift Registers | 176 |
| 7.20 | 74595 Shift Register | 176 |
| | References for Further Study | 180 |
| 8 | Frequency Division with Flip Flops | 181 |
| 8.1 | Introduction | 181 |
| 8.2 | Frequency Division with D Flip Flop | 181 |
| 8.3 | Frequency Division with 4017 | 186 |
| 8.4 | Frequency Division with 7490 | 191 |
| 8.5 | Frequency Division with 555 | 195 |
| | References for Further Study | 196 |
| 9 | Counter Circuits | 197 |
| 9.1 | Introduction | 197 |
| 9.2 | Low Frequency Clock Pulse Generation | 197 |
| 9.3 | Single Clock Pulse Generation | 199 |
| 9.4 | 4-Bit Binary Counter | 203 |
| 9.5 | 8-Bit Binary Counter | 205 |
| 9.6 | 14-Bit Binary Counter | 208 |
| 9.7 | 4-Bit Up/Down Counter | 210 |

| | | |
|-----------|---|------------|
| 9.8 | CMOS Counter/Divider | 215 |
| | References for Further Study | 221 |
| 10 | Oscillator Circuits | 223 |
| 10.1 | Introduction | 223 |
| 10.2 | Square Wave Generation with Transistor | 225 |
| 10.3 | Square Wave Generation with 555 IC | 227 |
| 10.4 | Square Wave Generation with NOT Gates | 228 |
| 10.5 | Pulse Generation with 555 IC | 230 |
| 10.6 | Non Retriggerable Monostable with 555 IC | 232 |
| 10.7 | Non Retriggerable Monostable with 74121 IC | 236 |
| 10.8 | Servomotor Tester with 555 IC | 237 |
| | References for Further Study | 239 |
| 11 | Analog-to-Digital and Digital-to-Analog Converters | 241 |
| 11.1 | Introduction | 241 |
| 11.2 | Analog to Digital Conversion with ADC0804 | 243 |
| 11.3 | Increasing the Analog to Conversion Accuracy | 245 |
| 11.4 | Voltage Level Monitor | 246 |
| 11.5 | Digital to Analog Conversion with DAC0808 | 248 |
| | References for Futher Study | 251 |